

1. What is a decoder? What is the relationship between its inputs and outputs? Derive the function(s) that maps inputs and outputs for a 2-to-4 decoder. Write a VHDL code that implements the 2-to-4 decoder using case statement.
 - a. A decoder is a popular combinational logic. It converts an input binary number into one high output.
 - b. If there are n-inputs, there will be 2^n outputs.
 - c. Truth Table

| a | b |
|-----------|-------------------|
| $i_1 i_0$ | $d_0 d_1 d_2 d_3$ |
| 00 | 1000 |
| 01 | 0100 |
| 10 | 0010 |
| 11 | 0001 |

- d. Functions: $d_0 = \bar{i}_1 \bar{i}_0$ and $d_1 = \bar{i}_1 i_0$ and $d_2 = i_1 \bar{i}_0$ and $d_3 = i_1 i_0$
- e. VHDL code with case statement

```
LIBRARY ieee ;
```

```
USE ieee.std_logic_1164.all ;
```

```
ENTITY dec2to4 IS
```

```
    PORT (a : IN STD_LOGIC_VECTOR(1 DOWNTO 0) ;
```

```
          b : OUT STD_LOGIC_VECTOR(3 DOWNTO 0) ) ;
```

```
END dec2to4 ;
```

```
ARCHITECTURE Behavior OF dec2to4 IS
```

```
BEGIN
```

```
    PROCESS(a)
```

```
    BEGIN
```

```
        CASE a IS
```

```
            WHEN "00" => b <= "1000";
```

```
            WHEN "01" => b <= "0100";
```

```
            WHEN "10" => b <= "0010";
```

```
            WHEN "11" => b <= "0001";
```

```
        END CASE;
```

```
    END PROCESS;
```


END Behavior ;

2. Implement the function $F(A, B, C, D) = A\bar{B} + \bar{A}B + A\bar{D} + A\bar{C}$ using a 4-to-16 decoder.

a. Truth Table

| ABCD | $F(A, B, C, D) = A\bar{B} + \bar{A}B + A\bar{D} + A\bar{C}$ |
|------|---|
| 0000 | 0 |
| 0001 | 0 |
| 0010 | 0 |
| 0011 | 0 |
| 0100 | 1 |
| 0101 | 1 |
| 0110 | 1 |
| 0111 | 1 |
| 1000 | 1 |
| 1001 | 1 |
| 1010 | 1 |
| 1011 | 1 |
| 1100 | 1 |
| 1101 | 1 |
| 1110 | 1 |
| 1111 | 0 |

b. Block diagram

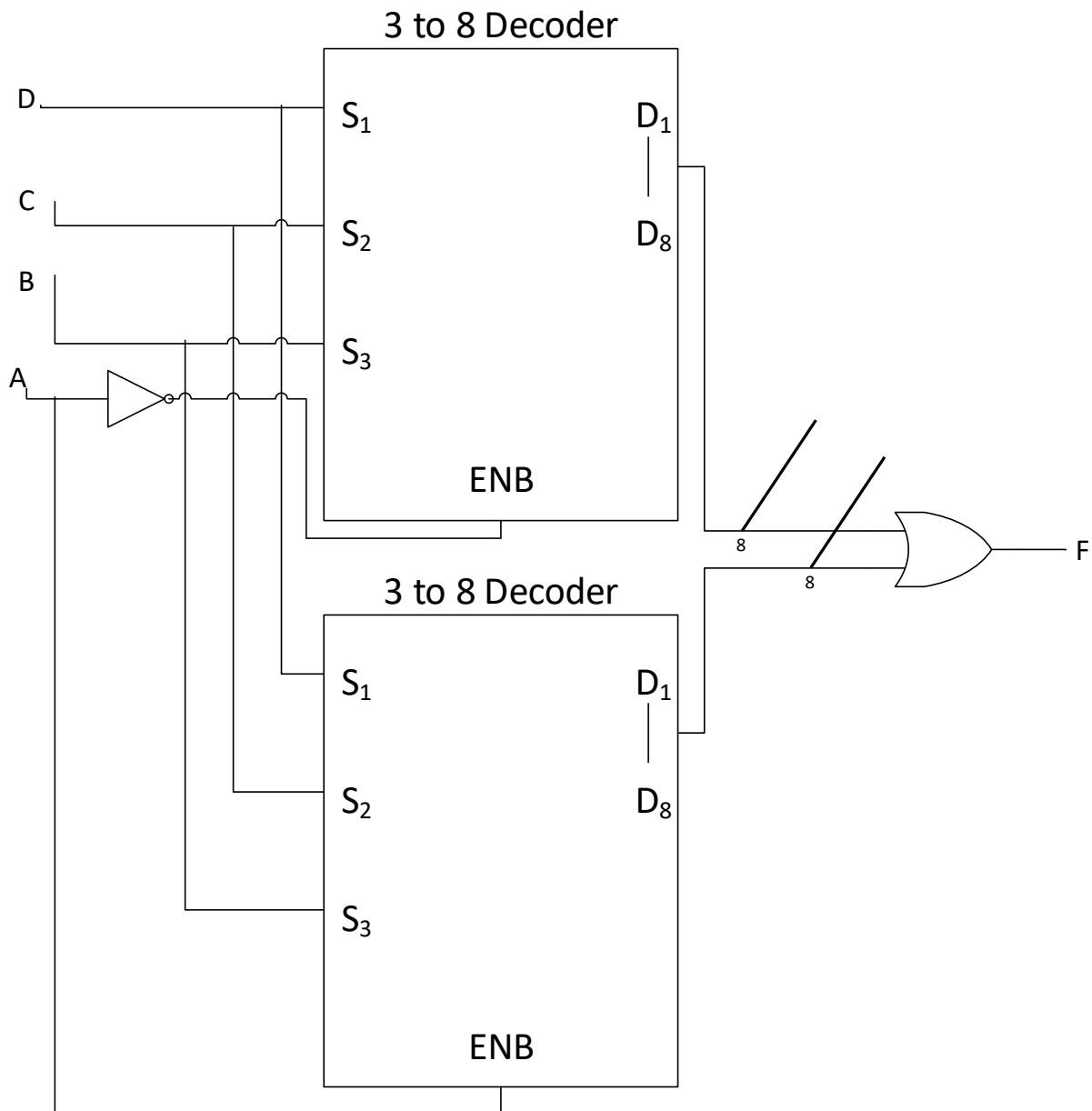

3. What is an encoder? What is the relationship between its inputs and outputs? Derive the function(s) that maps inputs and outputs for a 4-to-2 encoder. Write a VHDL code that implements the 4-to-2 encoder using case statement.
- An encoder is used to reduce the number of bits required to represent given information. Exactly one input is high.
 - When there are 2^n inputs, there are n outputs.
 - Truth Table

| a | b |
|-------------------|-----------|
| $w_3 w_2 w_1 w_0$ | $y_1 y_0$ |
| 0001 | 00 |
| 0010 | 01 |

| | |
|------|----|
| 0100 | 10 |
| 1000 | 11 |

- d. Functions: $w_3 = \overline{y_1} \overline{y_0}$ and $w_2 = \overline{y_1} y_0$ and $w_1 = y_1 \overline{y_0}$ and $w_0 = y_1 y_0$
e. VHDL code with case statement

LIBRARY ieee ;

USE ieee.std_logic_1164.all ;

ENTITY enc4to2 IS

PORT (a : IN STD_LOGIC_VECTOR(3 DOWNTO 0) ;

b : OUT STD_LOGIC_VECTOR(1 DOWNTO 0)) ;

END enc4to2 ;

ARCHITECTURE Behavior OF enc4to2 IS

BEGIN

PROCESS(a)

BEGIN

CASE a IS

WHEN "0001" => b <= "00";

WHEN "0010" => b <= "01";

WHEN "0100" => b <= "10";

WHEN "1000" => b <= "11";

END CASE;

END PROCESS;

END Behavior ;

4. What is a multiplexer? What is the relationship between its inputs and outputs? Derive the function(s) that maps inputs and outputs for a 4-to-1 multiplexer. Write a VHDL code that implements the 4-to-1 multiplexer using case statement.
- A multiplexer is another popular combinational building block. It routes one of its N data inputs to its one output, based on the binary value of select inputs.
 - With N inputs, there are $\log_2 N$ select lines. There is always one output.
 - Truth Table

| | | |
|------|---|--|
| ABCD | F | |
|------|---|--|

| | | |
|------|---|------------------|
| 0000 | 0 | F=D |
| 0001 | 1 | F=D |
| 0010 | 0 | F=D |
| 0011 | 1 | F=D |
| 0100 | 1 | $F=\overline{D}$ |
| 0101 | 0 | $F=\overline{D}$ |
| 0110 | 0 | F=0 |
| 0111 | 0 | F=0 |
| 1000 | 0 | F=0 |
| 1001 | 0 | F=0 |
| 1010 | 0 | F=D |
| 1011 | 1 | F=D |
| 1100 | 1 | F=1 |
| 1101 | 1 | F=1 |
| 1110 | 1 | F=1 |
| 1111 | 1 | F=1 |

- d. Functions: $F=D$ and $F=\overline{D}$ and $F=0$ and $F=1$
- e. VHDL code with Case statement

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mux4to1 IS
    PORT (a, b, c, d : IN STD_LOGIC;
          selection: IN STD_LOGIC_VECTOR(1 DOWNTO 0);
          f : OUT STD_LOGIC) ;
END mux4to1 ;

ARCHITECTURE Behavior OF mux4to1 IS
BEGIN
    PROCESS(a, b, c, d, selection)
    BEGIN
        CASE selection IS
            WHEN "00" => f <= a;
            WHEN "01" => f <= b;
            WHEN "10" => f <= c;
            WHEN OTHERS => f <= d;
```

END CASE;

END PROCESS;

END Behavior ;

5. Implement the function $F(A, B, C, D) = \Pi M(1, 2, 3, 4, 6, 8, 12, 14)$ using an 8-to-1 multiplexer.


a. Truth Table

| ABCD | $F(A, B, C, D) = \Pi M(1, 2, 3, 4, 6, 8, 12, 14)$ | |
|------|---|---------------|
| 0000 | 1 | $F = \bar{D}$ |
| 0001 | 0 | |
| 0010 | 0 | $F = 0$ |
| 0011 | 0 | |
| 0100 | 0 | $F = D$ |
| 0101 | 1 | |
| 0110 | 0 | $F = D$ |
| 0111 | 1 | |
| 1000 | 0 | $F = D$ |
| 1001 | 1 | |
| 1010 | 1 | $F = 1$ |
| 1011 | 1 | |
| 1100 | 0 | $F = D$ |
| 1101 | 1 | |
| 1110 | 0 | $F = D$ |
| 1111 | 1 | |

b. Use ABC as select lines. Function output varies between 1, 0, D, and \bar{D} .

c. Block diagram

8 to 1 MUX

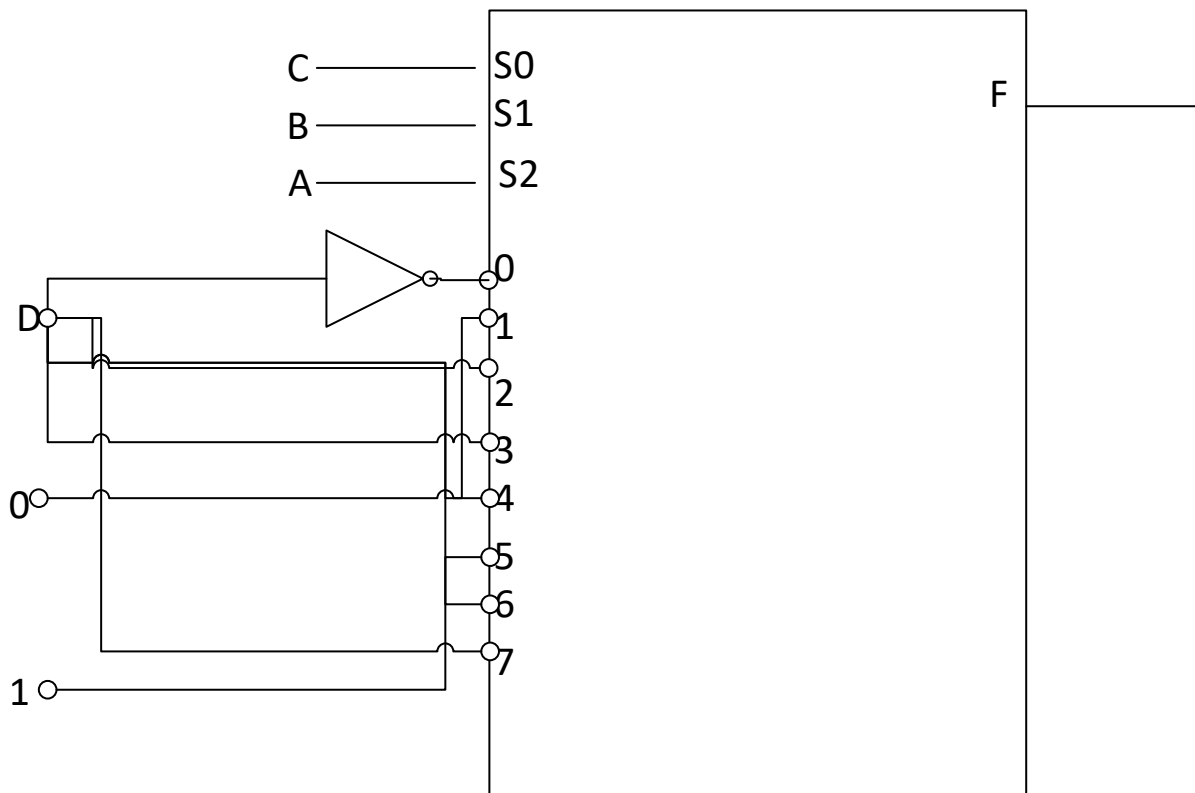

6. What is a demultiplexer? What is the relationship between its inputs and outputs? Derive the function(s) that maps inputs and outputs for a 1-to-4 demultiplexer.
- A demultiplexer routes a single input (if the enable is used as the input) to one of many outputs. Functions the same as a decoder.
 - With N outputs, there are $\log_2 N$ select lines. There is always one input.
 - Truth Table

| Data input | Select Inputs | | Outputs | | | |
|------------|---------------|-------|---------|-------|-------|-------|
| D | S_1 | S_0 | Y_3 | Y_2 | Y_1 | Y_0 |
| D | 0 | 0 | 0 | 0 | 0 | D |
| D | 0 | 1 | 0 | 0 | D | 0 |
| D | 1 | 0 | 0 | D | 0 | 0 |
| D | 1 | 1 | D | 0 | 0 | 0 |

- d. Functions: $Y_0 = D \overline{S_1} \overline{S_0}$ and $Y_1 = D \overline{S_1} S_0$ and $Y_2 = D S_1 \overline{S_0}$ and $Y_3 = D S_1 S_0$

$$F = D \overline{S_1} \overline{S_0} + D \overline{S_1} S_0 + D S_1 \overline{S_0} + D S_1 S_0$$

7. Derive the truth table for half-subtractor and full-subtractor. Derive the input-output function from the truth table.
- Truth Table half-subtractor

| Inputs | Outputs |
|--------|-----------------------------------|
| A B | D_i (Difference) B_0 (Borrow) |
| 0 0 | 0 0 |
| 0 1 | 1 1 |
| 1 0 | 1 0 |
| 1 1 | 0 0 |


- b. Half-subtractor input-output functions: $D_i = \bar{A}B + A\bar{B}$ and $B_0 = \bar{A}B$
c. Truth Table full-subtractor

| A | B | C | BORROW | DIFFERENCE |
|---|---|---|--------|------------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 |

- d. Full-subtractor input-output functions: $D_i = A \text{ xor } B \text{ xor } C$ and $B_0 = \overline{C(\bar{A} \text{ xor } B)} + \bar{A}B$
8. What is a multifunction register? Using block diagrams, implement a 3-bit multifunction register using D flip-flops and multiplexers that does parallel load, inverted parallel load, shift right, and shift left operations.
a. A multifunction register takes in parallel and serial input and outputs the operation done. Inputs must be specified to select which function will be used.
b. There will be 8 flip flops, but 3 unused.
c. Truth Table

| S2 | S1 | S0 | Operation |
|----|----|----|------------------------|
| 0 | 0 | 0 | Hold |
| 0 | 0 | 1 | Shift right |
| 0 | 1 | 0 | Shift left |
| 0 | 1 | 1 | Parallel load |
| 1 | 0 | 0 | Inverted parallel load |
| 1 | 0 | 1 | |
| 1 | 1 | 0 | |
| 1 | 1 | 1 | |

- d. Block diagram

 

9. Write a behavioral VHDL code that implements a 4-bit multifunction register that does parallel load, shift right, shift left, and rotate right operations. Write a VHDL test bench to test the operations with at least one test vector per operation.

a. VHDL code

```
LIBRARY ieee;

USE ieee.std_logic_1164.all;

ENTITY multfr IS
    PORT(Clock, shr_in, shl_in : IN STD_LOGIC;
          s : IN STD_LOGIC_VECTOR(1 DOWNTO 0);
          I : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
          Q : OUT STD_LOGIC_VECTOR(3 DOWNTO 0));
END multfr;

ARCHITECTURE behav OF multfr IS
    SIGNAL tmp: std_logic_vector(3 downto 0); -- 4-bit flip-flop
BEGIN
    PROCESS(Clock)
    BEGIN
        IF (clock' event and clock = '1') THEN
            CASE s IS
                when "00" => -- do nothing;
                when "01" => tmp <= I;
```

```
        when "10" =>
            tmp(0) <= tmp(1);
            tmp(1) <= tmp(2);
            tmp(2) <= tmp(3);
            tmp(3) <= shr_in;
        when "11" =>
            tmp(0) <= shl_in;
            tmp(1) <= tmp(0);
            tmp(2) <= tmp(1);
            tmp(3) <= tmp(2);
    END CASE;
END IF;
END PROCESS;

Q <= tmp;
END behav;
```

b. VHDL test bench

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;
LIBRARY UNISIM;
USE UNISIM.Vcomponents.ALL;
ENTITY problem9_tb IS
END problem9_tb;
ARCHITECTURE behavioral OF problem9_tb IS
    COMPONENT f2
        PORT( a, b, c : IN STD_LOGIC;
              f2 : OUT STD_LOGIC);
    END COMPONENT;
```

```
SIGNAL a, b, c, f2 : STD_LOGIC;

BEGIN

    UUT: f2 PORT MAP(

        a=>a,

        b => b,

        c => c,

        f2 => f2);

-- *** Test Bench - User Defined Section ***

tb : PROCESS

BEGIN

    a<='0'; b='0'; c='0';

    wait for 10 ms;

    a<='0'; b='0'; c='1';

    wait for 10 ms;

    a<='0'; b='1'; c='0';

    wait for 10 ms;

    a<='0'; b='1'; c='1';

    wait for 10 ms;

    a<='1'; b='0'; c='0';

    wait for 10 ms;

    a<='1'; b='0'; c='1';

    wait for 10 ms;

    a<='1'; b='1'; c='0';

    wait for 10 ms;

    a<='1'; b='1'; c='1';

    wait for 10 ms;

    WAIT; -- will wait forever

END PROCESS;
```

-- *** End Test Bench - User Defined Section ***

END behavioral;

10. What is a barrel shifter? Demonstrate how left shift by 9 positions is done using a 12- bit barrel shifter?

- A barrel shifter is a shifter that can shift by any amount.
- A 12-bit barrel shifter can shift left by 0, 1, 2, 3, 4, 5, 6, 7, 8, 9, 10, or 11 positions
- Chain four shifters: 8, 4, 2, and 1
- Can achieve any shift of 0 to 11 by enabling the correct combination of those four shifters, because the shifts should sum to the desired amount
- WXYZ = 1001 will do a shift left by 9 because it uses the 8 shifter and the 1 shifter.

| | | | |
|---|----|------|--------|
| Chain carries the 12 bits to next shifter: 0000 0011 0100 0111 | | | |
| W → 1 | Sh | << 8 | in ← 0 |
| Chain carries the 12 bits to next shifter: 0100 0111 0000 0000 (by 8) | | | |
| X → 0 | Sh | << 4 | in ← 0 |
| Chain carries the 12 bits to next shifter: 0100 0111 0000 0000 | | | |
| Y → 0 | Sh | << 2 | in ← 0 |
| Chain carries the 12 bits to next shifter: 0100 0111 0000 0000 | | | |
| Z → 1 | Sh | << 1 | in ← 0 |
| Chain carries the 12 bits to next shifter: 1000 1110 0000 0000 (by 1) | | | |
| Result: shift by 9: 1000 1110 0000 0000 | | | |

11. Differentiate (at least two differences) between a serial and an array multiplier.

- Serial Multiplier
 - Power used is minimal
 - Area used is minimal
 - Delay is longer
- Array Multiplier
 - An efficient layout of a combinational multiplier
 - Uses n-1 adders, eliminates registers
 - May be pipelined to decrease clock period at the expense of latency
 - Consumes a high amount of power
 - Takes up a lot of area